

**Lab 9-10 – Nano processor Design Competition**  
**CS1050 Computer Organization and Digital Design**

Group Members: -

- **Guruge S.M.L – 210201F**
- **Gunathunga W.S.D – 210196P**

➤ **Lab Task**

- The objective of this task is to design a 4-bit processor capable of executing the following 4 instructions.
  1. MOVI R, d - Move immediate value d to register R.
  2. ADD Ra, Rb - Add values in register Ra & Rb and store the result in Ra.
  3. NEG R - 2's complement of register R.
  4. JZR R, d - Jump if value in register R is 0.
- To build a certain processor, following components should be designed first.
  1. 4-bit Add/Subtract Unit
  2. 3-bit Adder
  3. 3-bit Program Counter
  4. 2-way 3-bit Multiplexer
  5. 2-way 4-bit Multiplexer
  6. 8-way 4-bit Multiplexer
  7. Register Bank
  8. Program ROM
  9. Instruction Decoder
  10. Slow Clock
- After Creating above components, we tested their functionalities using simulation codes.
- Then we connected these components using busses.
- Finally, we tested their functionalities using BASYS3 board.

➤ **Assembly program**

```
MOVI R1,1      ; R1 ← 1
MOVI R2,2      ; R2 ← 2
MOVI R3,3      ; R3 ← 3
MOVI R7,0      ; R7 ← 0
ADD R7,R1      ; R7 ← R7 + R1
ADD R7,R2      ; R7 ← R7 + R2
ADD R7,R3      ; R7 ← R7 + R3
JZR R0,7       ; If R0 = 0 jump to line 7
```

➤ **Machine code**

- 100010000001
- 100100000010
- 100110000011
- 101110000000
- 001110010000
- 001110100000
- 001110110000
- 110000000111

➤ **All VHDL Codes**

❖ Source Codes

• **4- bit adder subtracter**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity AdderSubtractor is
    Port ( A : in STD_LOGIC_Vector(3 downto 0);
          B : in STD_LOGIC_vector(3 downto 0);
          C_in : in STD_LOGIC_vector(1 downto 0);
          S : out STD_LOGIC_vector(3 downto 0);
          C_out : out STD_LOGIC;
          Zero : out std_logic;
          C_out_plus : out std_logic);
end AdderSubtractor;
architecture Behavioral of AdderSubtractor is
    component FA
    port (
        A: in std_logic;
        B: in std_logic;
        C_in: in std_logic;
        S: out std_logic;
        C_out: out std_logic);
    end component;
```

```

    SIGNAL FA0_S, FA0_C, FA1_S, FA1_C, FA2_S, FA2_C, FA3_S, FA3_C , output,
    C_tmp : std_logic;
    signal B_out,S0 : std_logic_vector(3 downto 0);
    begin
    B_out(0) <= (C_in(0) and (not C_in(1))) xor B(0);
    B_out(1) <= (C_in(0) and (not C_in(1))) xor B(1);
    B_out(2) <= (C_in(0) and (not C_in(1))) xor B(2);
    B_out(3) <= (C_in(0) and (not C_in(1))) xor B(3);

    C_tmp <= (C_in(0) and (not C_in(1)));

    FA_0 : FA
    port map (
        A => A(0),
        B => B_out(0),
        C_in => C_tmp,
        S => S0(0),
        C_Out => FA0_C);
    FA_1 : FA
    port map (
        A => A(1),
        B => B_out(1),
        C_in => FA0_C,
        S => S0(1),
        C_Out => FA1_C);
    FA_2 : FA
    port map (
        A => A(2),
        B => B_out(2),
        C_in => FA1_C,
        S => S0(2),
        C_Out => FA2_C);
    FA_3 : FA
    port map (
        A => A(3),
        B => B_out(3),
        C_in => FA2_C,
        S => S0(3),
        C_Out => output);
    C_Out <= C_tmp AND (output xor FA2_C) ;
    C_out_plus<= output and not(C_tmp);
    Zero <= (NOT(C_in(1) OR C_in(0))) AND (not(S0(0) or S0(1) or S0(2) or S0(3)));
    S<= S0;

```

- **3 – bit adder**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity adder_3_bit is
    Port ( A : in STD_LOGIC_Vector(2 downto 0);
          S : out STD_LOGIC_vector(2 downto 0));
end adder_3_bit;
```

architecture Behavioral of adder\_3\_bit is

```
component FA
port (
A: in std_logic;
B: in std_logic;
C_in: in std_logic;
S: out std_logic;
C_out: out std_logic);
end component;
```

```
SIGNAL FA0_C, FA1_C, FA2_C : std_logic;
begin
```

```
FA_0 : FA
port map (
    A => A(0),
    B => '1',
    C_in => '0',
    S => S(0),
    C_Out => FA0_C);
```

```
FA_1 : FA
port map (
    A => A(1),
    B => '0',
    C_in => FA0_C,
    S => S(1),
    C_Out => FA1_C);
```

```
FA_2 : FA
port map (
    A => A(2),
    B => '0',
    C_in => FA1_C,
    S => S(2),
    C_Out => FA2_C);
end Behavioral;
```

- **3 – bit program counter**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity program_Counter is
    Port ( D : in STD_LOGIC_VECTOR (2 downto 0);
          Reset : in STD_LOGIC:= '0';
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC_vector(2 downto 0):= "000");
end program_Counter;
```

architecture Behavioral of program\_Counter is

```
begin
    process(Clk) begin
        if(rising_edge(Clk)) then
            if Reset = '1' then
                Q <= "000";
            else
                Q <= D;
            end if;
        end if;
    end process;
```

end Behavioral;

- **2 – way 3 – bit Multiplexer**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity MUX_2_way_3_bit is
    Port ( I0 : in STD_LOGIC_VECTOR (2 downto 0);
          I1 : in STD_LOGIC_VECTOR (2 downto 0);
          D : out STD_LOGIC_VECTOR (2 downto 0);
          S : in STD_LOGIC);
end MUX_2_way_3_bit;
```

architecture Behavioral of MUX\_2\_way\_3\_bit is  
Signal Z1,Z2,Z3,Z4,Z5,Z6 : STD\_LOGIC;

begin

```
Z1 <= (I0(0) AND not S);
Z2 <= (I1(0) AND S);
```

```

Z3 <= (I0(1) AND not S);
Z4 <= (I1(1) AND S);
Z5 <= (I0(2) AND not S);
Z6 <= (I1(2) AND S);

```

```

D(0) <= Z1 OR Z2;
D(1) <= Z3 OR Z4;
D(2) <= Z5 OR Z6;

```

```

end Behavioral;

```

- **2 – way 4- bit Multiplexer**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity MUX_2_way_4_bit is
    Port ( I0 : in STD_LOGIC_VECTOR (3 downto 0);
          I1 : in STD_LOGIC_VECTOR (3 downto 0);
          D : out STD_LOGIC_VECTOR (3 downto 0);
          S : in STD_LOGIC);
end MUX_2_way_4_bit;

```

```

architecture Behavioral of MUX_2_way_4_bit is
    Signal Z1,Z2,Z3,Z4,Z5,Z6,Z7,Z8 : STD_LOGIC;

```

```

begin

```

```

Z1 <= (I0(0) AND not S);
Z2 <= (I1(0) AND S);
Z3 <= (I0(1) AND not S);
Z4 <= (I1(1) AND S);
Z5 <= (I0(2) AND not S);
Z6 <= (I1(2) AND S);
Z7 <= (I0(3) AND not S);
Z8 <= (I1(3) AND S);

```

```

D(0) <= Z1 OR Z2;
D(1) <= Z3 OR Z4;
D(2) <= Z5 OR Z6;
D(3) <= Z7 OR Z8;

```

```

end Behavioral;

```

- **8 – way 4-bit Multiplexer**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity MUX_8_way_4_bit is
    Port ( I0 : in STD_LOGIC_VECTOR (3 downto 0);
          I1 : in STD_LOGIC_VECTOR (3 downto 0);
          I2 : in STD_LOGIC_VECTOR (3 downto 0);
          I3 : in STD_LOGIC_VECTOR (3 downto 0);
          I4 : in STD_LOGIC_VECTOR (3 downto 0);
          I5 : in STD_LOGIC_VECTOR (3 downto 0);
          I6 : in STD_LOGIC_VECTOR (3 downto 0);
          I7 : in STD_LOGIC_VECTOR (3 downto 0);
          D : out STD_LOGIC_VECTOR (3 downto 0);
          S : in STD_LOGIC_VECTOR (2 downto 0);
          En : in std_logic);
end MUX_8_way_4_bit;
```

architecture Behavioral of MUX\_8\_way\_4\_bit is

Component Mux\_8\_1

```
port( S : in STD_LOGIC_VECTOR (2 downto 0);
      D : in STD_LOGIC_VECTOR (7 downto 0);
      EN : in STD_LOGIC;
      Y : out STD_LOGIC);
end component;
```

begin

Mux\_0:Mux\_8\_1

port map(

S => S,

D(0) => I0(0),

D(1) => I1(0),

D(2) => I2(0),

D(3) => I3(0),

D(4) => I4(0),

D(5) => I5(0),

D(6) => I6(0),

D(7) => I7(0),

Y => D(0),

EN => En

);

Mux\_1:Mux\_8\_1

port map(

S => S,

```
D(0) => I0(1),  
D(1) => I1(1),  
D(2) => I2(1),  
D(3) => I3(1),  
D(4) => I4(1),  
D(5) => I5(1),  
D(6) => I6(1),  
D(7) => I7(1),  
Y => D(1),  
EN => En
```

```
);  
Mux_2:Mux_8_1  
port map(  
S => S,  
D(0) => I0(2),  
D(1) => I1(2),  
D(2) => I2(2),  
D(3) => I3(2),  
D(4) => I4(2),  
D(5) => I5(2),  
D(6) => I6(2),  
D(7) => I7(2),  
Y => D(2),  
EN => En
```

```
);  
Mux_3:Mux_8_1  
port map(  
S => S,  
D(0) => I0(3),  
D(1) => I1(3),  
D(2) => I2(3),  
D(3) => I3(3),  
D(4) => I4(3),  
D(5) => I5(3),  
D(6) => I6(3),  
D(7) => I7(3),  
Y => D(3),  
EN => En
```

```
);
```

```
end Behavioral;
```



- **Register Bank**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity Register_Bank is
    Port ( Clk : in STD_LOGIC;
          Reg_En : in STD_LOGIC_VECTOR (2 downto 0);
          D : in STD_LOGIC_VECTOR (3 downto 0);
          S_out_0 : out STD_LOGIC_VECTOR (3 downto 0);
          S_out_1 : out STD_LOGIC_VECTOR (3 downto 0);
          S_out_2 : out STD_LOGIC_VECTOR (3 downto 0);
          S_out_3 : out STD_LOGIC_VECTOR (3 downto 0);
          S_out_4 : out STD_LOGIC_VECTOR (3 downto 0);
          S_out_5 : out STD_LOGIC_VECTOR (3 downto 0);
          S_out_6 : out STD_LOGIC_VECTOR (3 downto 0);
          S_out_7 : out STD_LOGIC_VECTOR (3 downto 0);
          reset : in std_logic);
end Register_Bank;
```

architecture Behavioral of Register\_Bank is

component Decoder\_3\_to\_8

```
Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
      EN : in STD_LOGIC;
      Y : out STD_LOGIC_VECTOR (7 downto 0));
```

end component;

component Reg

```
Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
      En : in STD_LOGIC;
      Clk : in STD_LOGIC;
      Q : out STD_LOGIC_VECTOR (3 downto 0);
      reset : in std_logic);
```

end component;

signal out\_Dec : std\_logic\_vector(7 downto 0);

begin

```
Decoder_3_to_8_0 : Decoder_3_to_8
    port map(
        I => Reg_En ,
        EN => '1',
        Y => out_Dec);
```

```
Reg_0 :Reg
  port map(
    reset => reset,
    D => D,
    En => out_Dec(0),
    Clk => Clk,
    Q => S_out_0);
Reg_1 :Reg
  port map(
    reset => reset,
    D => D,
    En => out_Dec(1),
    Clk => Clk,
    Q => S_out_1);
Reg_2 :Reg
  port map(
    reset => reset,
    D => D,
    En => out_Dec(2),
    Clk => Clk,
    Q => S_out_2);
Reg_3 :Reg
  port map(
    reset => reset,
    D => D,
    En => out_Dec(3),
    Clk => Clk,
    Q => S_out_3);
Reg_4 :Reg
  port map(
    reset => reset,
    D => D,
    En => out_Dec(4),
    Clk => Clk,
    Q => S_out_4);
Reg_5 :Reg
  port map(
    reset => reset,
    D => D,
    En => out_Dec(5),
    Clk => Clk,
    Q => S_out_5);
Reg_6 :Reg
  port map(
```

```

        reset => reset,
        D => D,
        En => out_Dec(6),
        Clk => Clk,
        Q => S_out_6);
Reg_7 :Reg
    port map(
        reset => reset,
        D => D,
        En => out_Dec(7),
        Clk => Clk,
        Q => S_out_7);

```

end Behavioral;

- **Program Rom**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.numeric_std.all;

```

entity ROM is

```

    Port ( address : in STD_LOGIC_VECTOR (2 downto 0);
          data : out STD_LOGIC_VECTOR (11 downto 0));
end ROM;

```

architecture Behavioral of ROM is

type rom\_type is array (0 to 7) of std\_logic\_vector(11 downto 0);

```

signal program_ROM : rom_type := (
    "100010000001", --MOVI R1,1
    "100100000010", --MOVI R2,2
    "100110000011", --MOVI R3,3
    "101110000000", --MOVI R7,0
    "001110010000", --ADD R7,R1
    "001110100000", --ADD R7,R2
    "001110110000", --ADD R7,R3
    "110000000111" --JZR R0,7

```

```

);
begin
data <= program_ROM(to_integer(unsigned(address)));

```

end Behavioral;

- **Instruction Decoder**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Instruction_Decoder is
    Port ( data : in STD_LOGIC_VECTOR (11 downto 0);
          Reg_check_jump : in STD_LOGIC_VECTOR(3 downto 0);
          Reg_En : out STD_LOGIC_VECTOR (2 downto 0);
          Reg_Sel_A : out STD_LOGIC_VECTOR (2 downto 0);
          Load_sel : out STD_LOGIC;
          Immediate_val : out STD_LOGIC_VECTOR (3 downto 0);
          Reg_Sel_B : out STD_LOGIC_VECTOR (2 downto 0);
          Add_Sub_Sel : out STD_LOGIC_VECTOR(1 downto 0);
          Jump_Flag : out STD_LOGIC;
          Address_To_Jump : out STD_LOGIC_VECTOR (2 downto 0));
end Instruction_Decoder;
```

architecture Behavioral of Instruction\_Decoder is

```
begin
    Reg_En <= data(9 downto 7);
    Reg_Sel_A <= data(9 downto 7);
    Reg_Sel_B <= data(6 downto 4);
    Load_Sel <= data(11)and not(data(10));
    Immediate_val <= data(3 downto 0);
    Add_Sub_Sel <= data(11 downto 10);
    --Jump_Flag <= ((NOT Reg_check_jump(0)) AND (NOT Reg_check_jump(1))
    AND (NOT Reg_check_jump(2)) AND (NOT Reg_check_jump(3))) AND data(11)
    AND data(10);
    Jump_Flag <= NOT( Reg_check_jump(0) Or Reg_check_jump(1) OR
    Reg_check_jump(2) OR Reg_check_jump(3)) AND data(11) AND data(10);
    Address_To_Jump <= data(2 downto 0);

end Behavioral;
```

- **Slow Clock**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Slow_clk is
    Port ( Clk_in : in STD_LOGIC;
```

```

        Clk_out : out STD_LOGIC);
end Slow_clk;

architecture Behavioral of Slow_clk is
    signal count: integer:=1;
    signal clk_status: std_logic:='0';

begin

    process(Clk_in)
    begin
        if(rising_edge(Clk_in)) then
            count<=count+1;
            if(count = 1) then
                clk_status <= not(clk_status);
                Clk_out <= clk_status;
                count<=1;
            end if;
        end if;
    end process;

end Behavioral;

```

- **Nano Processor**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity NanoProcessor is
    port(Clk : in STD_LOGIC;
         Reset : in STD_LOGIC;

```

```

        Reg7_Seg : out STD_LOGIC_VECTOR (6 downto 0);
        Zero : out STD_LOGIC;
        Overflow : out STD_LOGIC;
        Reg7_out : out std_logic_vector(3 downto 0);
        Anode : out std_logic_vector(3 downto 0));

end NanoProcessor;

architecture Behavioral of NanoProcessor is
component Slow_clk Port ( Clk_in : in STD_LOGIC;
        Clk_out : out STD_LOGIC);
end component;

component Register_Bank port(
        reset : in std_logic;
        Clk : in STD_LOGIC;
        Reg_En : in STD_LOGIC_VECTOR (2 downto 0);
        D : in STD_LOGIC_VECTOR (3 downto 0);
        S_out_0 : out STD_LOGIC_VECTOR (3 downto 0);
        S_out_1 : out STD_LOGIC_VECTOR (3 downto 0);
        S_out_2 : out STD_LOGIC_VECTOR (3 downto 0);
        S_out_3 : out STD_LOGIC_VECTOR (3 downto 0);
        S_out_4 : out STD_LOGIC_VECTOR (3 downto 0);
        S_out_5 : out STD_LOGIC_VECTOR (3 downto 0);
        S_out_6 : out STD_LOGIC_VECTOR (3 downto 0);
        S_out_7 : out STD_LOGIC_VECTOR (3 downto 0));
end component;

component MUX_2_way_3_bit Port(
        I0 : in STD_LOGIC_VECTOR (2 downto 0);
        I1 : in STD_LOGIC_VECTOR (2 downto 0);
        S : in STD_LOGIC;
        D : out STD_LOGIC_VECTOR (2 downto 0));
end component;

component Instruction_Decoder
Port ( data : in STD_LOGIC_VECTOR (11 downto 0);
        Reg_check_jump : in STD_LOGIC_VECTOR(3 downto 0);
        Reg_En : out STD_LOGIC_VECTOR (2 downto 0);
        Reg_Sel_A : out STD_LOGIC_VECTOR (2 downto 0);
        Load_sel : out STD_LOGIC;
        Immediate_val : out STD_LOGIC_VECTOR (3 downto 0);
        Reg_Sel_B : out STD_LOGIC_VECTOR (2 downto 0);
        Add_Sub_Sel : out STD_LOGIC_VECTOR(1 downto 0);
        Jump_Flag : out STD_LOGIC;

```

```
        Address_To_Jump : out STD_LOGIC_VECTOR (2 downto 0));  
end component;
```

```
component MUX_2_way_4_bit Port(  
    I0 : in STD_LOGIC_VECTOR (3 downto 0);  
    I1 : in STD_LOGIC_VECTOR (3 downto 0);  
    S : in STD_LOGIC;  
    D : out STD_LOGIC_VECTOR (3 downto 0));  
end component;
```

```
component Mux_8_Way_4_Bit port(  
    I0 : in STD_LOGIC_VECTOR (3 downto 0);  
    I1 : in STD_LOGIC_VECTOR (3 downto 0);  
    I2 : in STD_LOGIC_VECTOR (3 downto 0);  
    I3 : in STD_LOGIC_VECTOR (3 downto 0);  
    I4 : in STD_LOGIC_VECTOR (3 downto 0);  
    I5 : in STD_LOGIC_VECTOR (3 downto 0);  
    I6 : in STD_LOGIC_VECTOR (3 downto 0);  
    I7 : in STD_LOGIC_VECTOR (3 downto 0);  
    D : out STD_LOGIC_VECTOR (3 downto 0);  
    S : in STD_LOGIC_VECTOR (2 downto 0);  
    En : in std_logic);  
end component;
```

```
component ROM  
Port ( address : in STD_LOGIC_VECTOR (2 downto 0);  
      data : out STD_LOGIC_VECTOR (11 downto 0));  
end component;
```

```
component adder_3_bit port(  
    A : in STD_LOGIC_VECTOR (2 downto 0);  
    S : out STD_LOGIC_VECTOR (2 downto 0)  
);  
end component;
```

```
component AdderSubtracter  
Port ( A : in STD_LOGIC_VECTOR (3 downto 0);  
      B : in STD_LOGIC_VECTOR (3 downto 0);  
      C_in : in STD_LOGIC_VECTOR(1 downto 0);  
      S : out STD_LOGIC_VECTOR (3 downto 0);  
      C_out : out STD_LOGIC;  
      Zero : out Std_logic;  
      C_out_plus : out std_logic);  
end component;
```

```
component program_Counter  
Port ( D : in STD_LOGIC_VECTOR (2 downto 0);  
      Q : out STD_LOGIC_VECTOR (2 downto 0);  
end component;
```

```

        Clk : in STD_LOGIC;
        Reset : in STD_LOGIC);

end component;

component LUT_16_7
    port( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : out STD_LOGIC_VECTOR (6 downto 0));
end component;

signal
Reg_En0,Mux0_Out,Mux0_I0,Mux0_I1,Reg_Sel_Out_A,Reg_Sel_Out_B,Mem_Sel
I : STD_LOGIC_VECTOR (2 downto 0);
signal
Reg_In,Reg_Out_0,Reg_Out_1,Reg_Out_2,Reg_Out_3,Reg_Out_4,Reg_Out_5,Reg_Out_6,Reg_Out_7,Reg_Check_In,Im_Val, AddSubOut,Mux_B_Out:
STD_LOGIC_VECTOR (3 downto 0);
signal I_Dec_In : std_logic_vector(11 downto 0);
signal Mux0_Sel,I_Load_sel,slowClk, C_out_plus : std_logic;
signal AddSubSel : std_logic_vector(1 downto 0);

begin
    Anode <= "1110";
    Slow_Clock : Slow_clk

    Port map( Clk_in => Clk,
              Clk_out => slowClk );

    RegisterBank : Register_Bank
    port map(
        reset => Reset,
        Clk => slowClk,
        Reg_En => Reg_En0,
        D => Reg_In,
        S_out_0 => Reg_Out_0,
        S_out_1 => Reg_Out_1,
        S_out_2 => Reg_Out_2,
        S_out_3 => Reg_Out_3,
        S_out_4 => Reg_Out_4,
        S_out_5 => Reg_Out_5,
        S_out_6 => Reg_Out_6,
        S_out_7 => Reg_Out_7
    );

```



```

Mux_2_way_3_bit0 : MUX_2_way_3_bit
port map( I0 => Mux0_I0,
          I1 => Mux0_I1,
          S => Mux0_Sel,
          D => Mux0_Out
        );

InstructionDecorder : Instruction_Decoder
Port map(data => I_Dec_In,
          Reg_check_jump => Reg_Check_In,
          Reg_En => Reg_En0,
          Reg_Sel_A => Reg_Sel_Out_A,
          Load_sel => I_Load_sel,
          Immediate_val => Im_Val,
          Reg_Sel_B => Reg_Sel_Out_B,
          Add_Sub_Sel => AddSubSel,
          Jump_Flag => Mux0_Sel,
          Address_To_Jump => Mux0_I1);

```

```

Mux2Way4Bit : MUX_2_way_4_bit Port map(
          I0 => AddSubOut,
          I1 => Im_Val,
          S => I_Load_sel,
          D => Reg_In);

```

```

Mux8Way4Bit_1 : Mux_8_Way_4_Bit port map(
          I0 => Reg_Out_0,
          I1 => Reg_Out_1,
          I2 => Reg_Out_2,
          I3 => Reg_Out_3,
          I4 => Reg_Out_4,
          I5 => Reg_Out_5,
          I6 => Reg_Out_6,
          I7 => Reg_Out_7,
          D => Reg_Check_In,
          S => Reg_Sel_Out_A,
          En => '1');

```

```

Mux8Way4Bit_2 : Mux_8_Way_4_Bit port map(
          I0 => Reg_Out_0,
          I1 => Reg_Out_1,
          I2 => Reg_Out_2,
          I3 => Reg_Out_3,
          I4 => Reg_Out_4,
          I5 => Reg_Out_5,

```

```
I6 => Reg_Out_6,  
I7 => Reg_Out_7,  
D => Mux_B_Out,  
S => Reg_Sel_Out_B,  
En => '1');
```

```
ROM0 : ROM  
  Port map ( address => Mem_Sel,  
            data => I_Dec_In);
```

```
Adder: adder_3_bit  
  port map(  
    A => Mem_Sel,  
    S => Mux0_I0 );
```

```
Adder_Sub : AdderSubtractor  
  Port map ( A => Mux_B_Out,  
            B => Reg_Check_In,  
            C_in => AddSubSel,  
            S => AddSubOut,  
            C_out => Overflow,  
            Zero => Zero);
```

```
Program_Counter0 : program_Counter  
  Port map( D => Mux0_Out,  
           Q => Mem_Sel,  
           Clk => slowClk,  
           Reset => Reset);
```

```
S_Seg_Out : LUT_16_7  
  port map( address => Reg_Out_7,  
           data => Reg7_Seg);  
Reg7_out <= Reg_Out_7;
```

```
end Behavioral;
```


## ❖ Simulation Codes

You can get the respective simulation codes by following hyperlinks.


- [adder Subtractor TB](#)
- [3 - bit adder TB](#)
- [3 - bit program counter TB](#)
- [2-way 3-bit mux TB](#)
- [2-way 4-bit Mux TB](#)
- [8-way 4-bit Mux TB](#)
- [RegisterBank TB](#)
- [ROM TB](#)
- [Instruction Decoder TB](#)
- [NanoProcessor TB](#)

### ➤ Timing Diagrams


#### • Adder\_Subtractor

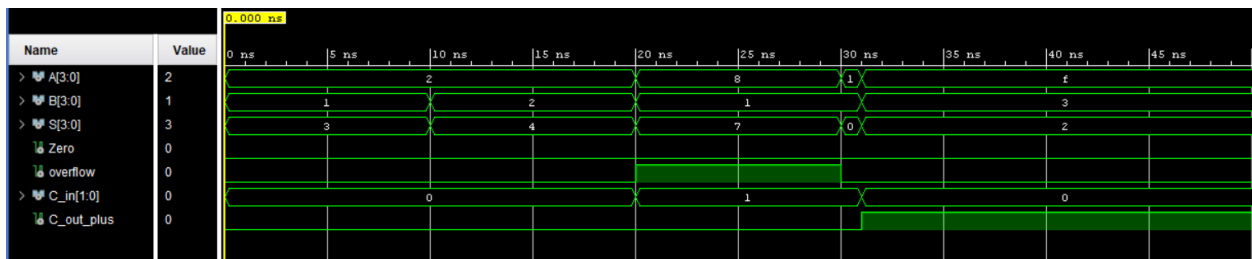


#### • 3-bit Adder

 


#### • 3- bit program counter

 


#### • 2-way 3-bit Multiplexer

 


- 2 - way 4- bit Multiplexer

 

- 8 – way 4- bit Multiplexer

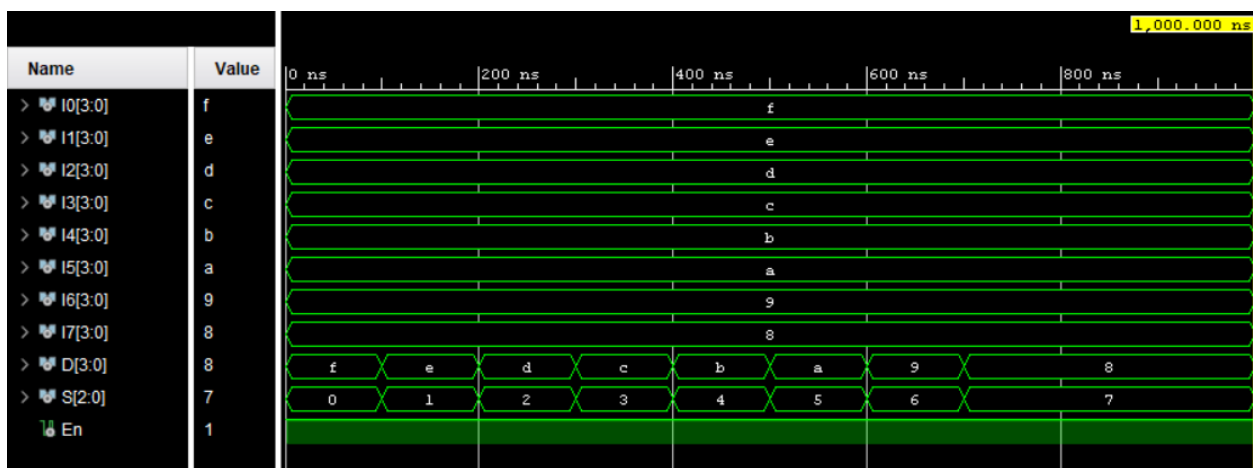


- Register Bank

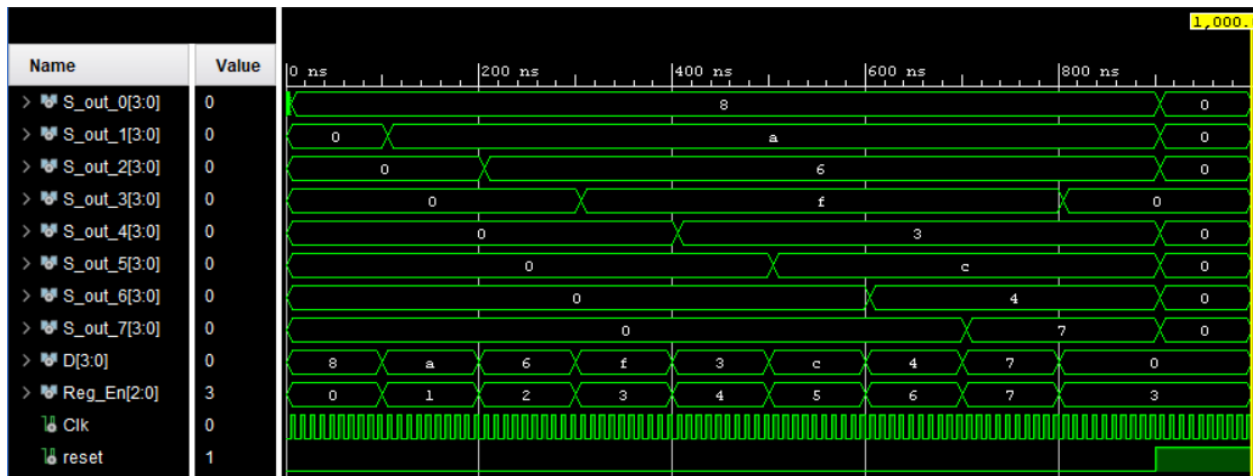


- Program Counter



- Instruction Decoder

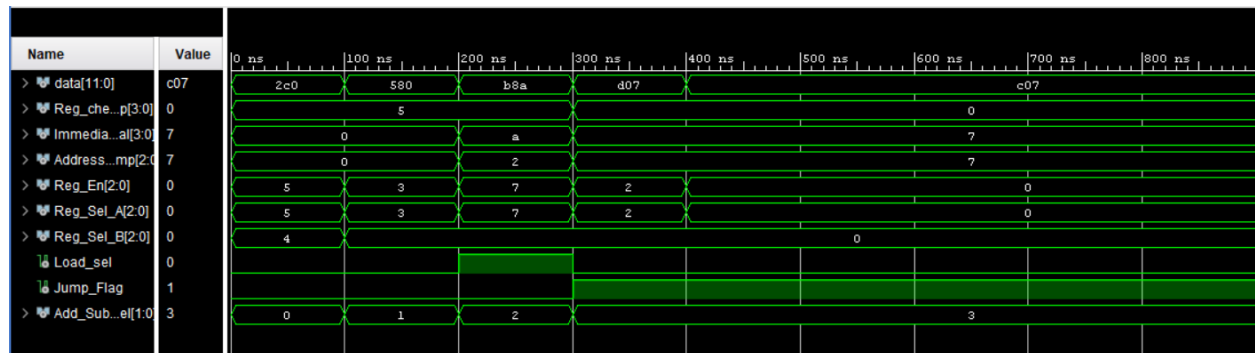

- Nano Processor

 

## ➤ Conclusion

- Using buses instead of many parallel wires simplifies the design process for a microprocessor in VHDL.
- Simulating and testing each component is critical to ensure the reliability and correctness of the final product.
- Building a microprocessor in VHDL provides an opportunity to gain a deeper understanding of the internal structure and operation of such devices.

- The project can help develop valuable teamwork skills as multiple individuals work together to create a complex system.
- The project requires hardcoding assembly instructions as binary values into ROM since microprocessors only understand machine language.
- From this project we learn how to debug, test, and optimize their circuit designs using simulation tools and on the development board.

➤ **Contribution Of Each Member**

Name	Designing Parts	No. Of Hours Spend
Guruge S.M.L	Instruction Decoder 8-way 4-bit Multiplexer 4-bit Add/Subtract Unit Program ROM Register Bank	12 Hours
Gunathunga W.S.D	2-way 3-bit Multiplexer 2-way 4-bit Multiplexer 3-bit Adder 3-bit Program Counter Clock Controller	12 Hours